

INDEX

Basic circuits, conductors and non-conductors

- ELI 001 Electrical circuits
- ELI 002 Double-throw switches
- ELI 004 Conductors and non-conductors - solids
- ELI 005 Voltage
- ELI 006 Voltage sources in series circuits
- ELI 007 Voltage sources in parallel circuits
- ELI 008 Terminal voltage
- ELI 009 Voltage drop across a light bulb
- ELI 010 Amperage
- ELI 011 Voltage sources in series circuits – short-circuit current
- ELI 012 Voltage sources in parallel circuits - short-circuit current
- ELI 013 Voltage sources in series circuits - amperage measurement
- ELI 014 Voltage sources in parallel circuits - amperage measurement
- ELI 017 The human body as an electrical conductor
- ELI 019 Closing a circuit by grounding - electrical resistance

Electrical resistance

- ELI 040 Light bulbs in parallel circuits (loads)
- ELI 041 Light bulbs in series circuits