

Electronics

Semiconductors – Resistors

- EOD 1.1 PTC resistor
- EOD 1.2 Automatic protection from overheating
- EOD 1.3 NTC resistor
- EOD 1.4 Model of an electric thermometer
- EOD 1.5 Photo resistor (LDR)
- EOD 1.6 Model of a light meter
- EOD 1.7 Varistor (VDR)
- EOD 1.8 Amperage across a VDR under AC

Diodes

- EOD 2.1 Silicon diode
- EOD 2.2 The silicon diode acts as a rectifier
- EOD 2.3 Characteristic curve of semiconducting diodes
- EOD 2.4 Basic materials: germanium and silicon
- EOD 2.5 Light-emitting diode (LED)
- EOD 2.6 Zener diode
- EOD 2.7 Zener diode under AC voltage
- EOD 2.8 Curve characteristic of the zener diode
- EOD 2.9 Protection against overloading
- EOD 2.10 Basic experiment for stabilizing voltage
- EOD 2.11 An Si-diode can protect from overloading
- EOD 2.12 Polarity tester

Transistors 1

- EOD 3.1.1 The transistor as a double diode (NPN)
- EOD 3.1.2 The transistor as a double diode (PNP)
- EOD 3.2.1 Base current lets collector current through (NPN)
- EOD 3.2.2 Base current lets collector current through (PNP)
- EOD 3.3 Only one power source for base and collector current
- EOD 3.4 Light sets off alarm
- EOD 3.5 Base voltage divider
- EOD 3.6 Burglar alarm with trip wire
- EOD 3.7 Automatic illumination
- EOD 3.8 Alarm using light barrier
- EOD 3.9 Fire detector
- EOD 3.10 Model of an electric thermometer
- EOD 3.11 Induction voltage controlling a transistor
- EOD 3.12 LF - Amplifier
- EOD 3.13 Microphone amplifier
- EOD 3.14 The conducting transistor

Capacitors

- EOD 4.1 A capacitor can store charges
- EOD 4.2 Direction of charging and discharging current
- EOD 4.3 Charging a capacitor
- EOD 4.4 Discharging a capacitor
- EOD 4.5 Capacitor supplies base current
- EOD 4.6 An uncharged capacitor acts as a short circuit
- EOD 4.7 Capacitor behaves unexpectedly
- EOD 4.8 Capacitor under AC voltage
- EOD 4.9 Capacitor as an alternating current resistor
- EOD 4.10 A capacitor separates dc voltage

Multivibrator Circuit

- EOD 5.1 Bistable multivibrator
- EOD 5.2 Support from a capacitor
- EOD 5.3 Monostable multivibrator
- EOD 5.4 Flashing circuit
- EOD 5.5 Astable multivibrator (functioning)
- EOD 5.6 Multivibrator music
- EOD 5.7 Light generates music
- EOD 5.8 Square and triangle generator

Rectifier Circuits

- EOD 6.1 Half-wave rectification
- EOD 6.2 Bridge rectifier 1
- EOD 6.3 Bridge rectifier 2
- EOD 6.4 Center-tap circuit
- EOD 6.5 The center-tap circuit in practice
- EOD 6.6 Doubling voltage

Transistors 2

- EOD 7.1 The transistor as a switch
- EOD 7.2 The transistor as a controllable resistor
- EOD 7.3 The transistor as an amplifier (emitter circuit)
- EOD 7.4 Setting the operating point
- EOD 7.5 Characteristic curve of a transistor
- EOD 7.6 The operating point needs to be set properly
- EOD 7.7 Negative feedback
- EOD 7.8 Base voltage and collector current
- EOD 7.9 Negative feedback in practice
- EOD 7.10 Common base circuit
- EOD 7.11 Collector circuit
- EOD 7.12 Stabilizing voltage supply
- EOD 7.13 Constant current source
- EOD 7.14 Constant current with two transistors

Thyristors

- EOD 8.1 A thyristor consists of four regions
- EOD 8.2 Thyristor under DC 1
- EOD 8.3 Thyristor gate conditions
- EOD 8.4 Thyristor under AC voltage
- EOD 8.5 Phase angle control
- EOD 8.6 Controlling power by triac
- EOD 8.7 Overload protection using a thyristor

Photoelectronics

- EOD 9.1 Light sets charge carriers free
- EOD 9.2 Solar cells connected parallel
- EOD 9.3 Solar cells connected in series
- EOD 9.4 Solar voltage dependent on angle of incidence and temperature
- EOD 9.5 Sensitive indicator for lighting changes
- EOD 9.6 Phototransistor
- EOD 9.7 Optically coupling electrical circuits
- EOD 9.10 Optocoupler
- EOD 9.11 DC circuit controls AC voltage
- EOD 9.12 Optocoupler controls higher voltage
- EOD 9.13 Fiber optic transmitter
- EOD 9.14 Fiber optic receiver
- EOD 9.15 Signal transmission through optical fiber
- EOD 9.16 Audio transmission through optical fiber

Transistor Circuits

- EOD 10.1 Darlington collector circuit
- EOD 10.2 Darlington emitter circuit
- EOD 10.3 Principle of the Darlington circuit
- EOD 10.4 The human body as a resistor
- EOD 10.5 Liquid level gauge
- EOD 10.6 Liquid level gauge with Darlington transistor
- EOD 10.7 Sensor contact
- EOD 10.8 Controlling mains voltage
- EOD 10.9 A simple light organ
- EOD 10.10 Transmission of music 1
- EOD 10.11 Transmission of music 2
- EOD 10.12 Two-stage transistor circuit
- EOD 10.13 Faulty light bulbs replaced automatically
- EOD 10.14 Universal alarm circuit
- EOD 10.15 Universal circuit using a thyristor
- EOD 10.16 Two-stage amplifier
- EOD 10.17 Direct coupling of amplifier stages